





7. Now, try Questions 1 through 6 using different resistors. Take a photo of your setup and test it. What did you observe?